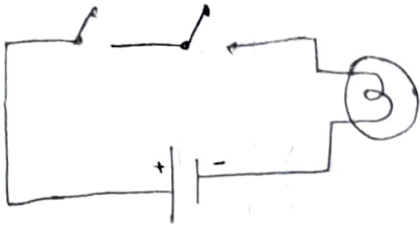



Programmable Logic Control

Logic Gates

1. AND Gate -




Circuit Diagram

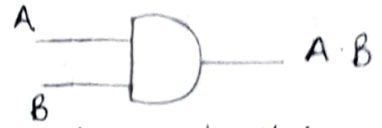



A	B	output
0	0	0
0	1	0
1	0	0
1	1	1

2. OR Gate -

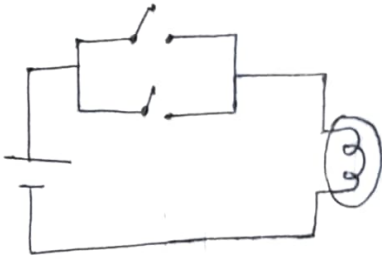


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

AND IN PLC Logic -

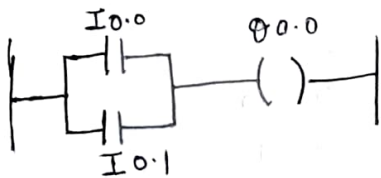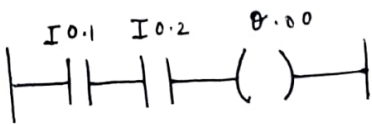


OR GATE

Q.1 $\rightarrow AB + CD = Y$

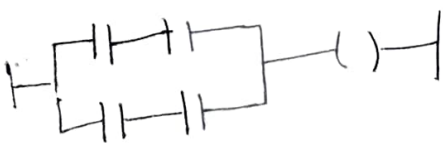

Q.2 $\rightarrow$

$A \Rightarrow Y = \bar{A}$	
0	1
1	0

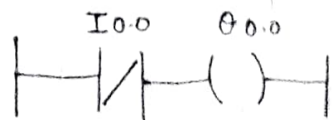



Circuit Diagram

Universal Gates


① NAND
② NOR

① NAND $\Rightarrow$ I/P = A, B
O/P = Y
 $Y = \overline{A \cdot B} = \bar{A} + \bar{B}$ (By De Morgan's theorem)

② NOR $\Rightarrow Y = \overline{A + B} = \bar{A} \cdot \bar{B}$

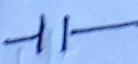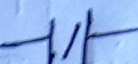A $\rightarrow$ 
 $\bar{A}$ $\rightarrow$ 
 $+$ $\rightarrow$ Parallel
 $\cdot$ $\rightarrow$ Series


Examples

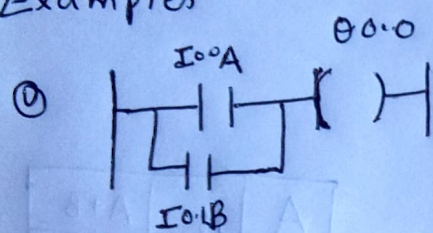

② NAND $\bar{A} \cdot \bar{B} = Y$
 $\bar{A} + \bar{B} = Y$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

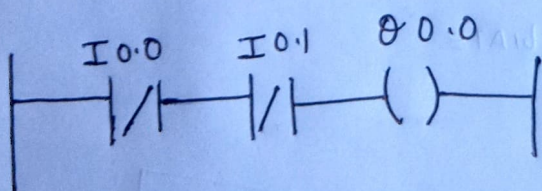③ NOR $Y = \overline{A + B} = \bar{A} \cdot \bar{B}$




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$\Rightarrow$ XOR & XNOR

XOR $\rightarrow \bar{A}B + A\bar{B}$

XNOR $\rightarrow AB + \bar{A}\bar{B}$

$$XOR \rightarrow \bar{A}B + A\bar{B}$$

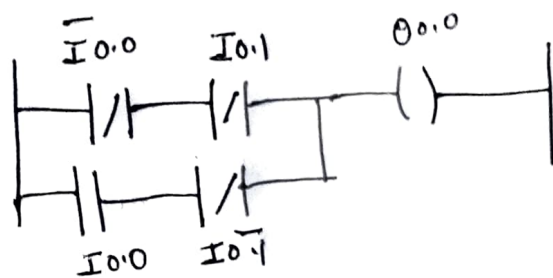

XNOR —

